
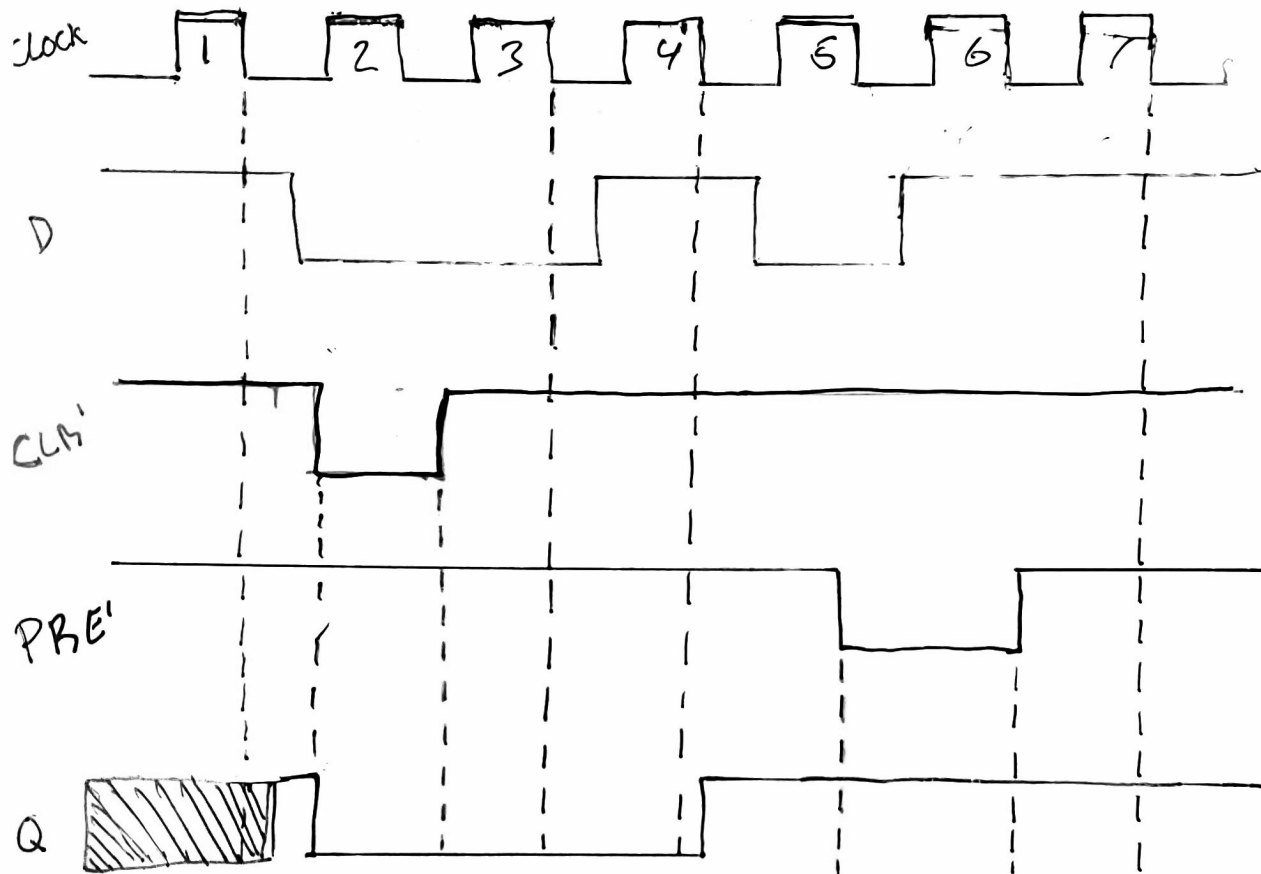


Chapter 6, problem 3c,d,e: For the input shown below,
show the flip flop outputs.

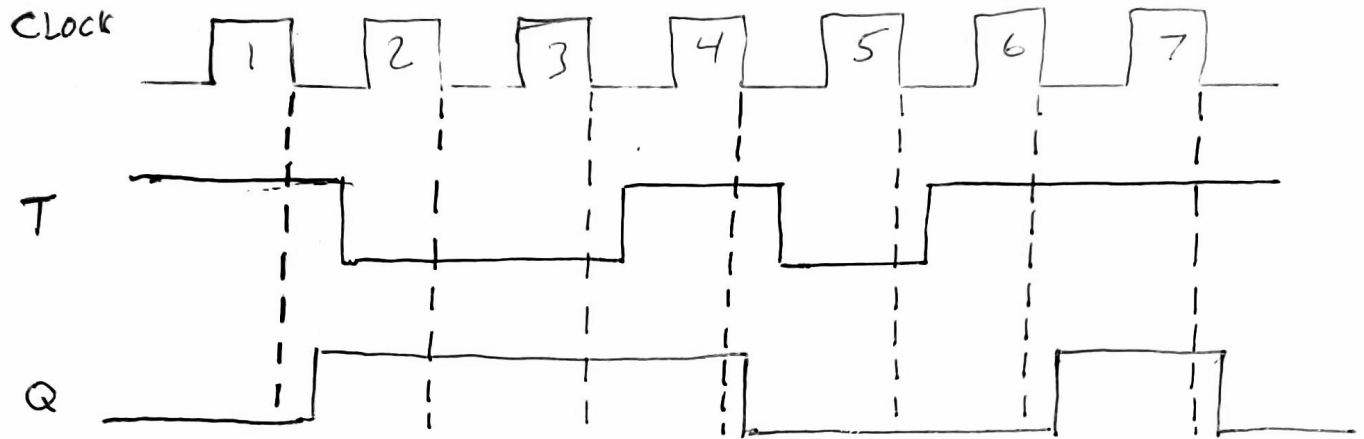
(C) Assume that the flip flop is a D flip flop with
active low clear.



- (d) Assume that the flip flop is a T flip flop with the same input as part a, and that Q is initially 0.




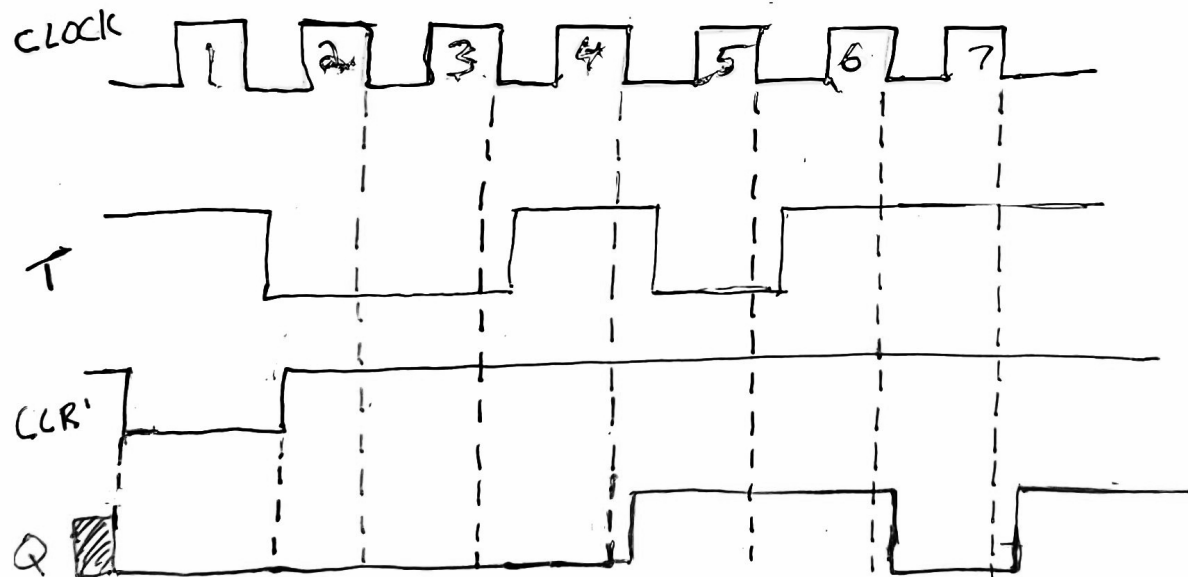- (e) Assume that the flip flop is a T flip flop with an active low clear and the same input as part b.




Chapter 6, problem 4: For a negative-edge triggered JK flip flop with active-low Preset and Clear inputs (74112), complete each individual timing diagram with the output Q.

(a)

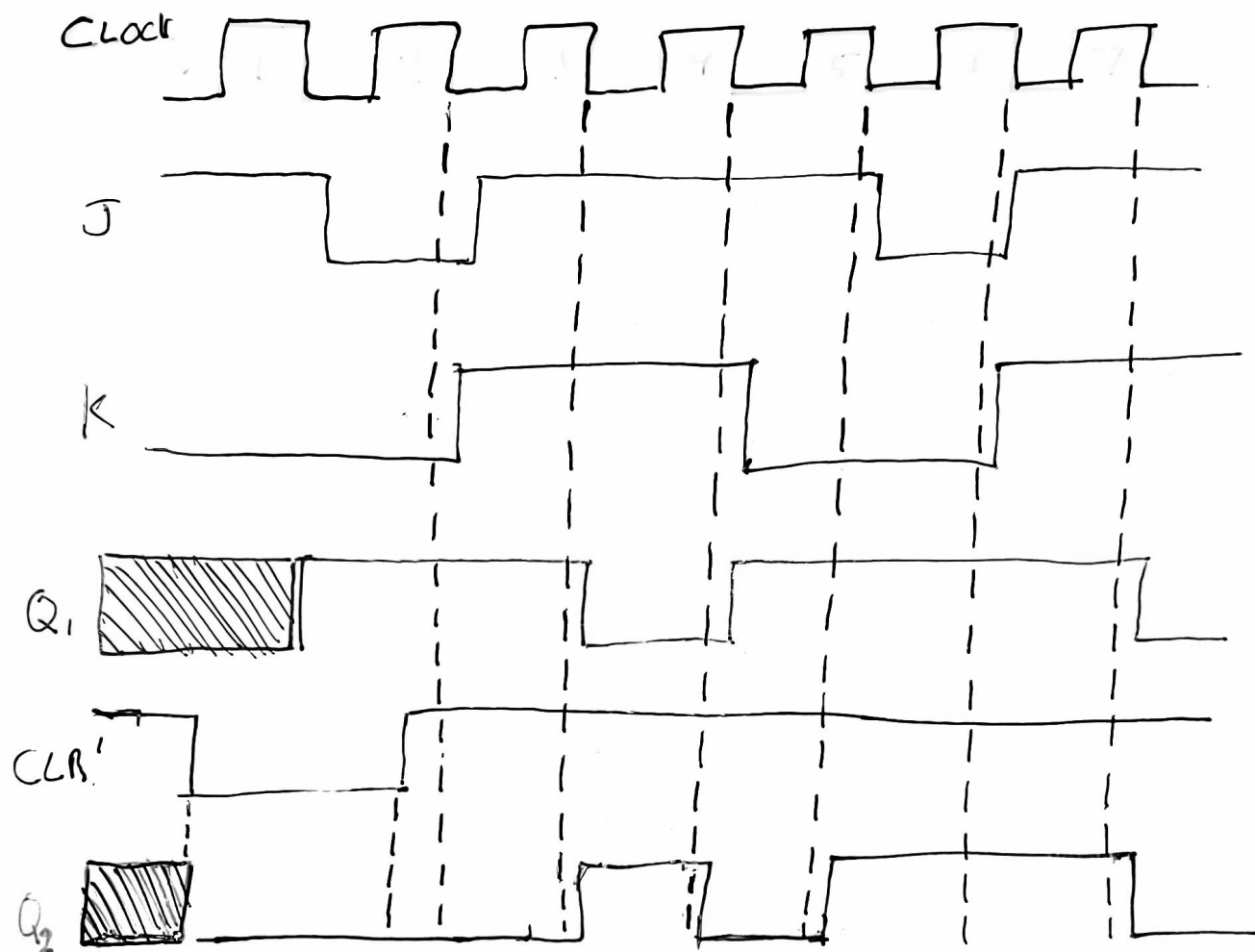


(b)

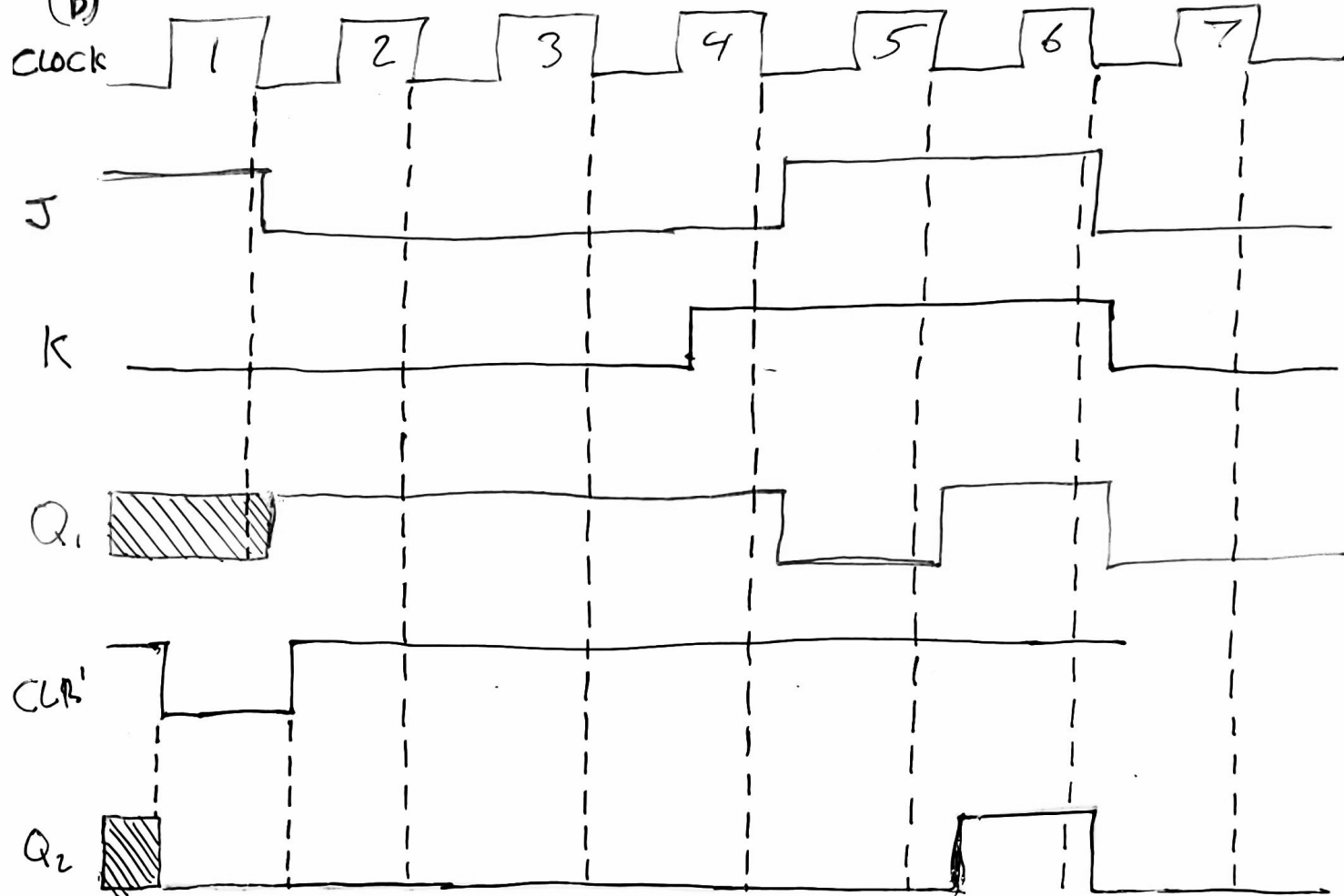


(c)


Clock

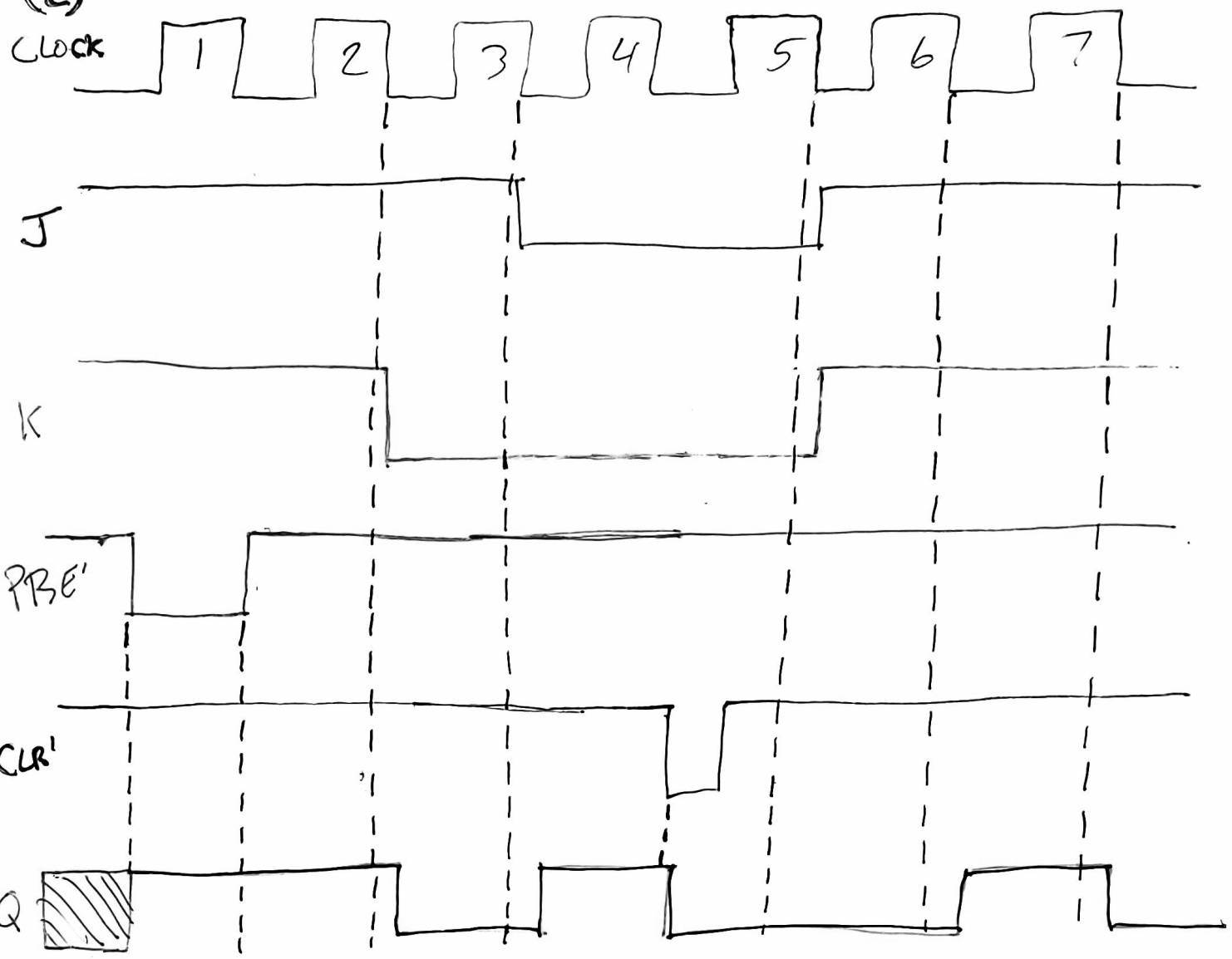

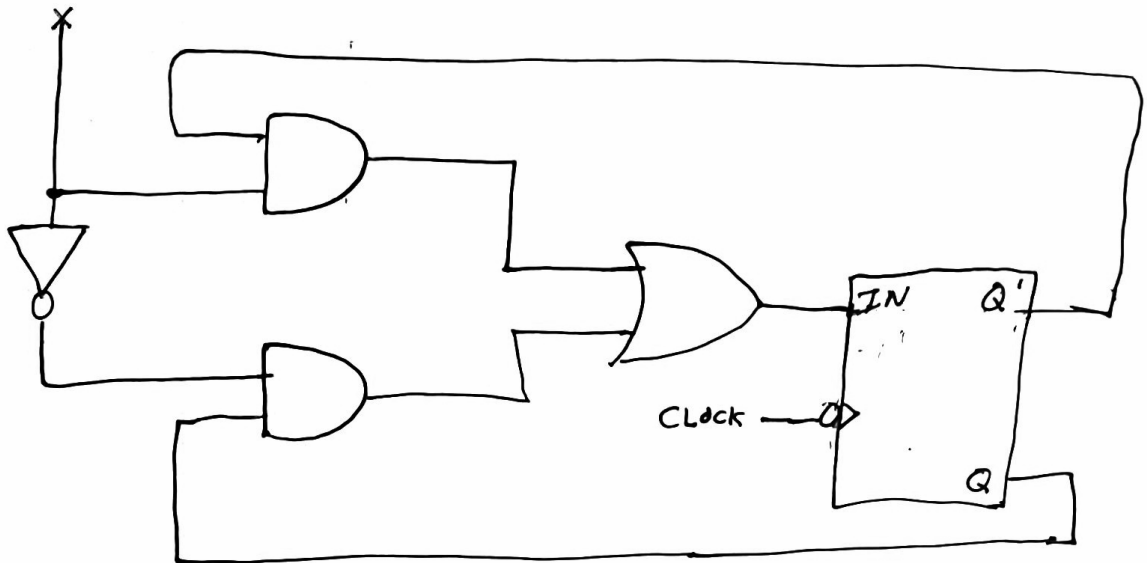Chapter 6, problem 5: Considering the following circuit, complete the timing diagram if the flip flop is:



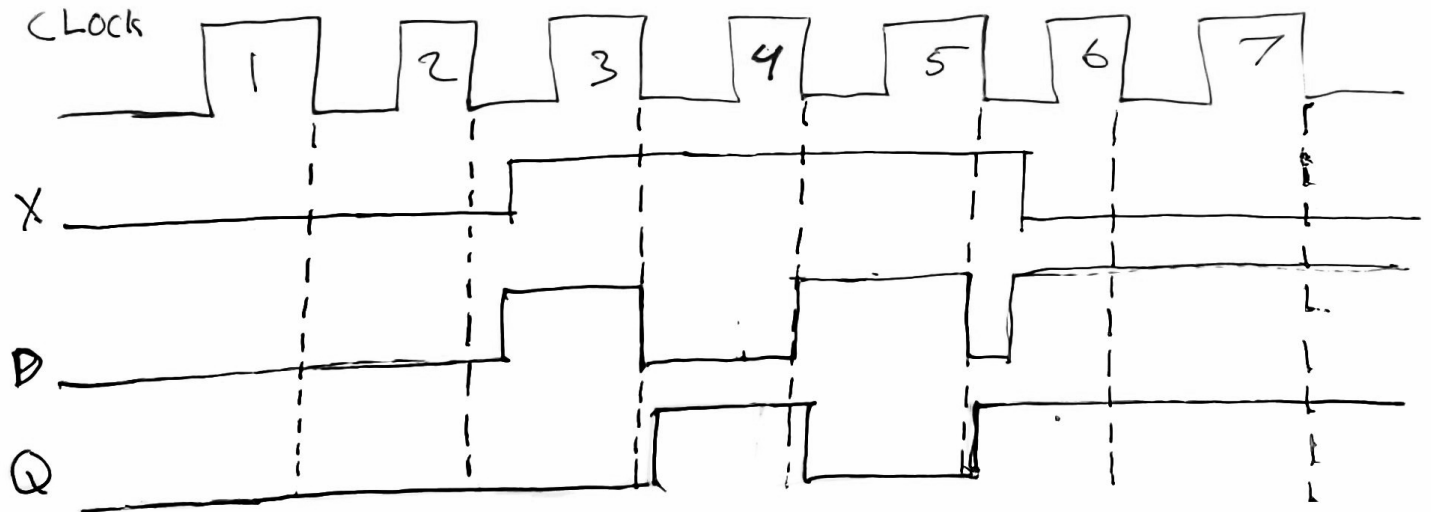
(a) a D flip flop (assume $Q = 0$ initially)



6


(b) A T flip flop (Assume $Q = 0$ initially)

CLOCK

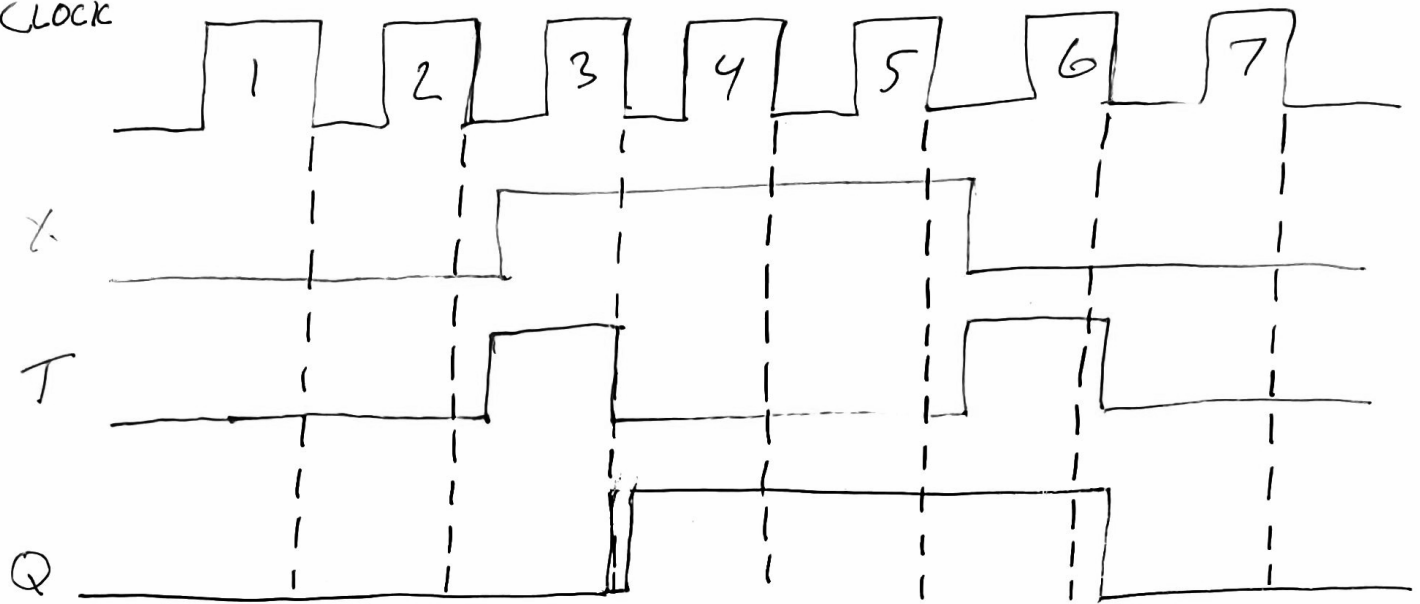

Chapter 6 problem 6: We have a new type of flip flop with inputs A and B. If $A = 0$, the $Q^* = B$; If $A = 1$, $Q^* = B'$

(a) Show a diagram for this flip flop

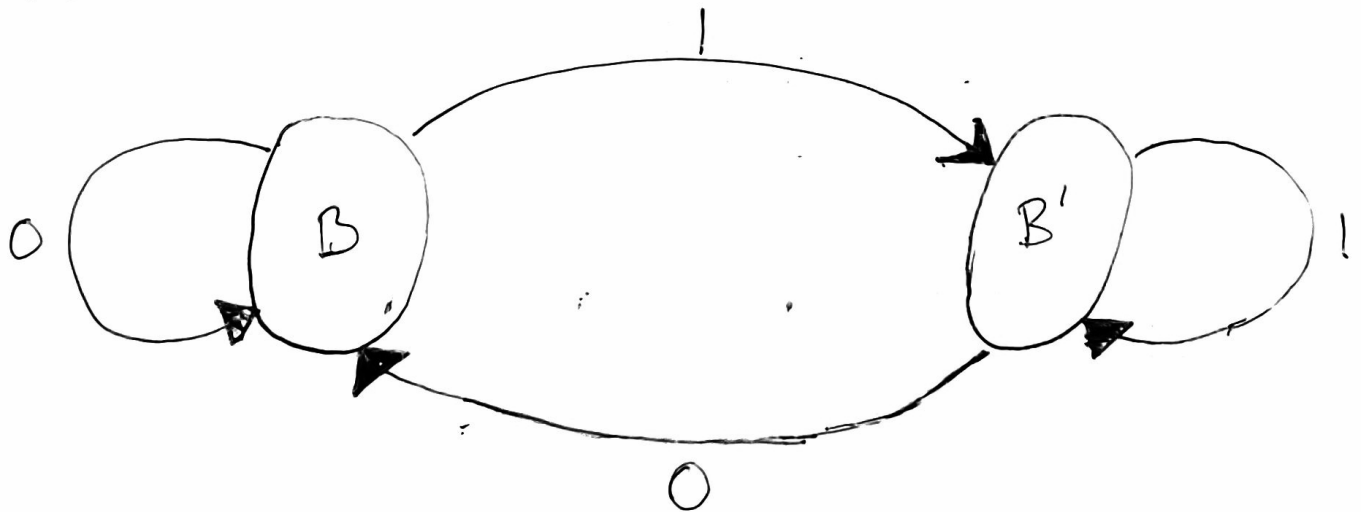

(b) Write an equation for Q^* in terms of A , B and Q .


A	B	Q	Q'
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Q \ AB				
	00	01	11	10
0		1		1
1		1		1

Q^*


Equation: $Q^* = A'B + AB'$

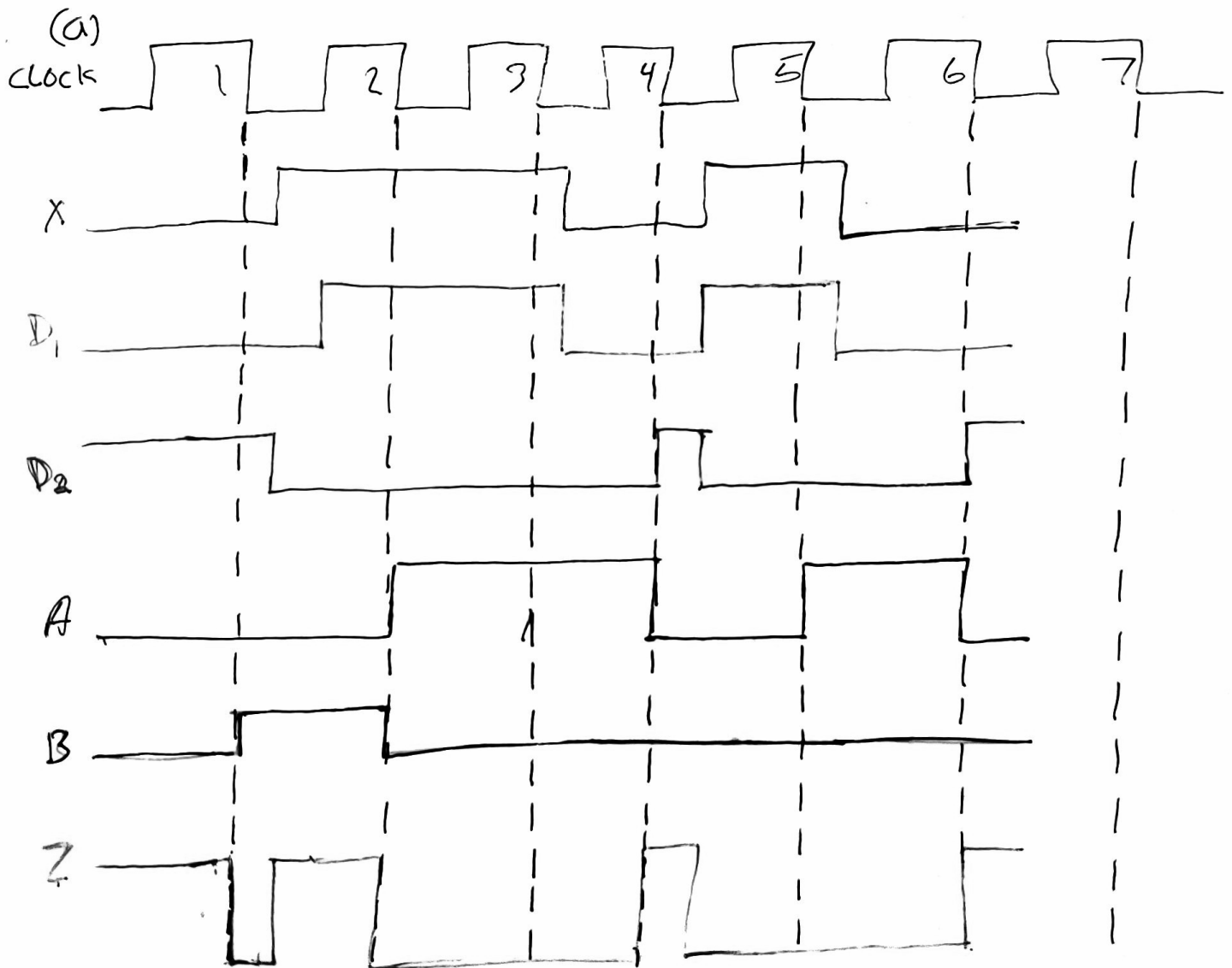Chapter 6, Problem 7: For each of the following circuits, complete the timing diagram for the state of each flip flop and the output, where shown. All flip flops are trailing-edge triggered. For those circuits in which there is no clear input, assume each flip flop starts at 0.



Chapter 6, problem 8: For the following circuit and input string:

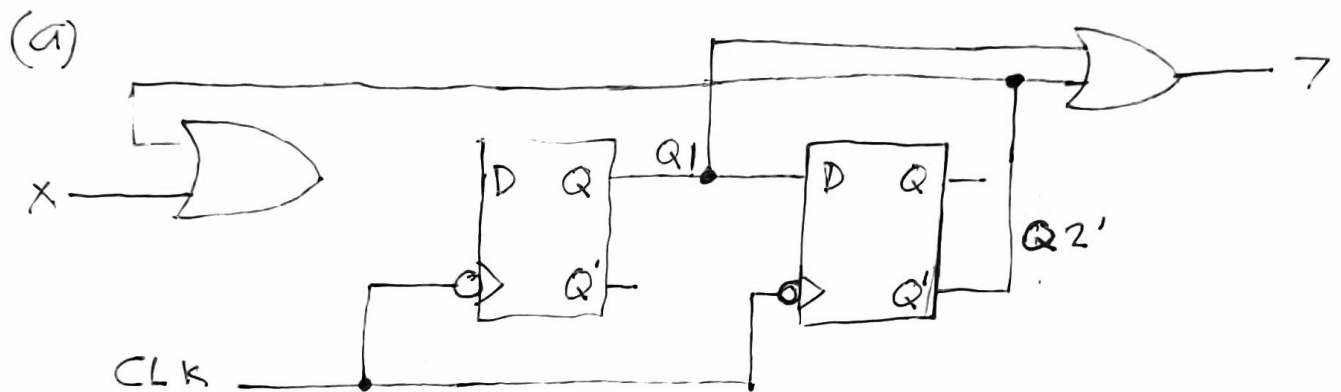- (i) Construct a state table (calling the states 00, 01, 10, 11)
- (ii) Show a timing trace for the flip-flops and the output as far as possible. Assume that the initial value of each flip flop is 0.



X 001100110

(i) State Table:

q_1, q_2	$q_1^* q_2^*$		Z
	X=0	X=1	
00	10	10	1
01	00	10	0
11	11	11	1
10	01	11	1

(ii) Timing Trace.

x	0	0	1	1	0	0	1	1	0				
q1	0	1	1	1	1	0	0	1	1	0	?	1	?
q2	0	0	1	1	1	1	0	0	1	1	0	?	1
z	1	1	1	1	1	0	1	1	1	0	1	1	?